

# Sequential Logic

How do we store a bit?



# Combinational vs. Sequential

- Combinational: output depends completely on the value of the inputs.
  - time doesn't matter.
- Sequential: output also depends on the *state a little while ago*.
  - can depend on the value of the output some time in the past.

# Memory


- Think about how you might design a combinational circuit that could be used as a single bit *memory*.
- Use your *memory* to recall that the output of a gate can change whenever the inputs change.

# Gate Timing

  

A	B	A nor B
0	0	1
0	1	0
1	0	0
1	1	0

# Feedback

 

What happens when A changes from 1 to 0?

- Try connecting the microphone input to the earphone output on your PC.
- Try holding a mirror in front of you while you are looking in a mirror.
- Try using [google.com](http://google.com) to search for the term “google”.


*Caution: the above experiments may result in opening a worm hole in your immediate surroundings!*

# Feedback can be stable

- It is possible to use feedback in a circuit that is predictable and *stable*.
- It is harder to tell what is going on (when compared to combinational circuits), but it is possible:
  - figure out what the output is at some initial time.
  - use that output to determine the next output.
  - continue until the worm hole contracts...


A	B	A nor B
0	0	1
0	1	0
1	0	0
1	1	0

# S-R latch

 



S stands for "Set" as in "Set to a 1"  
R stands for "Reset" (set to a 0).

# S-R latch Truth Table

 

$Q_t$	$S_t$	$R_t$	$Q_{t+1}$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	?
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	?

# S-R latch Timing

 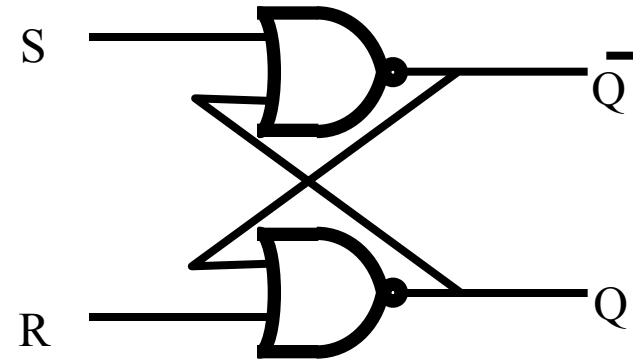


$\Delta t$  = One Gate Delay

# Clocked S-R Latch


- Inside a computer we want the output of gates to change only at specific times. All ops. in a computer are synchronized.
- We can add some circuitry to make sure that changes occur only at the *clock* edges (when the clock changes from 0 to 1).

# Clocked S-R Latch

 

- Q only changes when the Clock is a 1.
- If Clock is 0, neither S or R *reach* the NOR gates.
 
# Clocked SR Latch Timing Diagram example



1

# Characteristic table for clocked SR Latch

Characteristic Eqn:  $Q(t+1) = Q(t)(\text{not } R) + S$  &  $S * R = 0$

S(t)	R(t)	Q(t)	Q(t+1)	Condition
0	0	0	0	no change
0	0	1	1	nochange
0	1	0	0	reset to 0
0	1	1	0	reset to 0
1	0	0	1	set to 1
1	0	1	1	set to 1
1	1	0	---	forbidden
1	1	1	---	forbidden

Characteristic tables specify state of table after one clock pulse for given input and initial state.

## SR Latch, Excitation table

Q(t)	Q(t+1)	S(t)	R(t)
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

X above means “does not matter”


at the current i/p must be to obtain the  
positions  $Q(t) \rightarrow Q(t+1)$

# What if $S=R=1$ ?

- The truth table shows “--” when  $S=R=1$ .
- The value of  $Q$  is undetermined. The situation gets worse when  $SR=00$ : Both gates try and drive their outputs to 1. This results in a *race condition* ~ behavior of ckt. depends upon the relative transit times of the two signals over the combinatorial paths- The circuit is not *stable*
- Now that we have a clock we can make sure that we **PREVENT** the  $S=R=1$  condition.

# Avoiding $S=R=1$ : The D Latch

Clocked by definition.

 


D	Clock	$Q(t+1)$
X	0	$Q(t)$
0	1	0
1	1	1

Char. Eq.:  $Q(t+1) = D$


# D Latch

(D: Delay or Data)

 

- Now have only one input: D.
- If D is a 1 when the clock changes from 1 to 0, the circuit will *remember* the value 1 ( $Q=1$ ).
- If D is a 0 when the clock changes from 1 to 0, the circuit will *remember* the value 0 ( $Q=0$ ).

# D Latch Timing

 


# D Flip-Flops

Flip-flops: Sensitive to the clock edge.

When clock = 0, the slave latch is enabled and its o/p is equal the master o/p and the master latch is disabled.

 
When clock = 1, the master is enabled the data i/p is stored in the master latch. The slave however is disabled. Any changes in i/p change Q1, but the value at Q1 does not affect the slave o/p Q. When pulse returns to zero, the master is isolated from the input and the current value of Q1 is transferred to the o/p Q.



D	Clock	$Q(t+1)$
X	0	$Q(t)$
0	↓	0
1	↓	1
X	↑	$Q(t)$
 
# 8 Bit Memory

- We can use 8xD Flip-Flops to create an 8 bit memory.
- We have 8 inputs that we want to *store*, all are *written* at the same time.
  - all 8 flip-flops use the same clock.



# 8 Bit Memory

